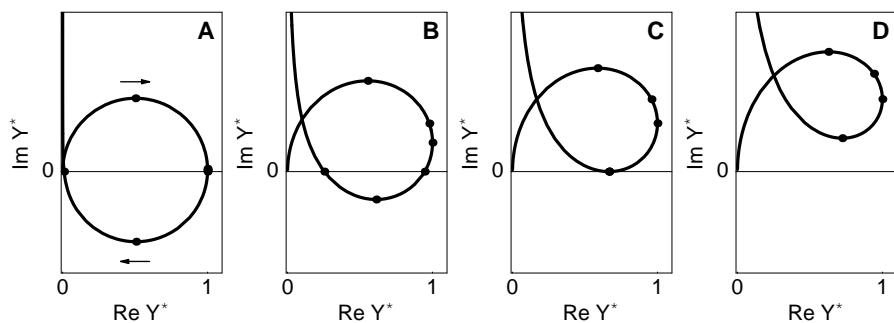


**Handbook
of
Electrochemical Impedance Spectroscopy**



**CIRCUITS
made of
RESISTORS, INDUCTORS and
CAPACITORS**

ER@SE/LEPMI
J.-P. Diard, B. Le Gorrec, C. Montella

Hosted by Bio-Logic @ www.bio-logic.info



August 31, 2011

Contents

1 Circuits made of R, L and C	5
1.1 (L+(R/C)) circuit	5
1.1.1 Circuit	5
1.1.2 Impedance	5
1.1.3 Reduced impedance	5
1.2 (R ₀ +(L+(R/C))) circuit	6
1.2.1 Impedance	7
1.2.2 Reduced impedance	7
1.3 (C+(R/L)) circuit	7
1.3.1 Circuit	7
1.3.2 Impedance	7
1.3.3 Reduced impedance	8
1.4 (R/L)+(R/C) circuit	9
1.4.1 Impedance	9
1.4.2 Reduced impedance	10
1.4.3 Nyquist impedance diagrams	10
1.4.4 Inductive and capacitive Nyquist diagrams	11
1.4.5 $\rho = R_1/R_2 = 1$	12
1.4.6 Array of Nyquist impedance diagrams	12
1.5 RLC parallel circuit	12
1.5.1 Circuit	12
1.5.2 Admittance	13
1.5.3 Reduced admittance	14
1.5.4 Impedance	14
1.5.5 Reduced impedance	14
1.6 RLC serie circuit	14
1.6.1 Circuit	14
1.6.2 Impedance	15
1.6.3 Reduced impedance	15
1.6.4 Admittance	15
1.6.5 Reduced admittance	16
1.7 R ₀ +RLC parallel circuit	16
1.7.1 Circuit	16
1.7.2 Impedance	16
1.8 Transformation formulae (R ₁ /L ₁)+(R ₁ /C ₂) → r ₁ + RLC parallel	17

2 Quartz resonator	19
2.1 BVD equivalent circuit	19
2.2 Admittance	19
2.3 Reduced admittance	19
2.3.1 Characteristic frequencies	20

Chapter 1

Circuits made of R, L and C

1.1 (L+(R/C)) circuit

1.1.1 Circuit

Fig. 1.1.

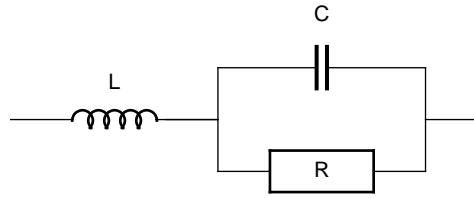


Figure 1.1: Circuit (L+(R/C)).

1.1.2 Impedance

$$Z(\omega) = L i \omega + \frac{R}{1 + R C i \omega}$$
$$\operatorname{Re} Z(\omega) = \frac{R}{C^2 R^2 \omega^2 + 1}, \quad \operatorname{Im} Z(\omega) = \omega \left(L - \frac{C R^2}{C^2 R^2 \omega^2 + 1} \right)$$

1.1.3 Reduced impedance

$$Z^*(u) = \frac{Z(u)}{R} = i T u + \frac{1}{1 + i u}, \quad u = R C \omega, \quad T = \frac{L}{C R^2} \quad (1.1)$$
$$\operatorname{Re} Z^*(u) = \frac{1}{u^2 + 1}, \quad \operatorname{Im} Z^*(u) = u \left(T - \frac{1}{u^2 + 1} \right)$$

Reduced characteristic angular frequency $u_c = 1$ with:

$$\operatorname{Re} Z(u_c) = 1/2, \quad \operatorname{Im} Z(u_c) = T - 1/2$$

$T < 1 \Rightarrow:$

- $u_{\text{Im } Z=0} = \sqrt{\frac{1-T}{T}}$, $\text{Re } Z(u_{\text{Im } Z=0}) = T$.

- reduced angular frequency at the apex :

$$u_a = \frac{1}{\sqrt{2}} \sqrt{\frac{-2T + \sqrt{8T+1} - 1}{T}}$$

with:

$$\begin{aligned} \text{Re } Z(u_a) &= \frac{1}{4} (\sqrt{8T+1} + 1) \\ \text{Im } Z(u_a) &= \frac{\sqrt{T} (\sqrt{8T+1} - 3) \sqrt{-2T + \sqrt{8T+1} - 1}}{\sqrt{2} (\sqrt{8T+1} - 1)} \end{aligned}$$

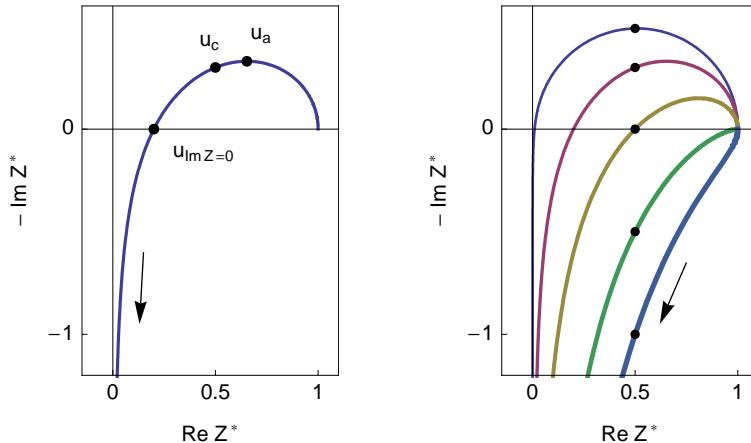


Figure 1.2: Nyquist diagram of the reduced impedance for the $(L+(R/C))$ circuit (Fig. 1.1, Eq. (1.2)) plotted for $T = 0.2$ (left) and $T = 0.01, 0.2, 0.5, 1, 1.5$ (right). The line thickness increases with increasing T . Dots: reduced characteristic angular frequency $u_c = 1$ (right).

1.2 $(R_0+(L+(R/C)))$ circuit

Fig. 1.3.

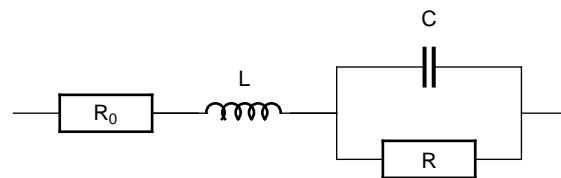


Figure 1.3: Circuit $(R_0+(L+(R/C)))$.

1.2.1 Impedance

$$Z(\omega) = R_0 + L i \omega + \frac{R}{1 + R C i \omega}$$

$$\operatorname{Re} Z(\omega) = R_0 + \frac{R}{C^2 R^2 \omega^2 + 1}, \quad \operatorname{Im} Z(\omega) = \omega \left(L - \frac{C R^2}{C^2 R^2 \omega^2 + 1} \right)$$

1.2.2 Reduced impedance

$$Z^*(u) = \frac{Z(u)}{R} = \rho + i T u + \frac{1}{1 + i u}, \quad u = R C \omega, \quad \rho = \frac{R_0}{R}, \quad T = \frac{L}{C R^2} \quad (1.2)$$

$$\operatorname{Re} Z^*(u) = \rho + \frac{1}{u^2 + 1}, \quad \operatorname{Im} Z^*(u) = u \left(T - \frac{1}{u^2 + 1} \right)$$

Reduced characteristic angular frequency $u_c = 1$ with:

$$\operatorname{Re} Z(u_c) = \rho + 1/2, \quad \operatorname{Im} Z(u_c) = T - 1/2$$

$T < 1 \Rightarrow$:

- $u_{\operatorname{Im} Z=0} = \sqrt{\frac{1-T}{T}}$, $\operatorname{Re} Z(u_{\operatorname{Im} Z=0}) = \rho + T$.

- reduced angular frequency at the apex :

$$u_a = \frac{1}{\sqrt{2}} \sqrt{\frac{-2T + \sqrt{8T+1}-1}{T}}$$

with:

$$\operatorname{Re} Z(u_a) = \rho + \frac{1}{4} \left(\sqrt{8T+1} + 1 \right)$$

$$\operatorname{Im} Z(u_a) = \frac{\sqrt{T} (\sqrt{8T+1}-3) \sqrt{-2T + \sqrt{8T+1}-1}}{\sqrt{2} (\sqrt{8T+1}-1)}$$

1.3 (C+(R/L)) circuit

1.3.1 Circuit

Fig. 1.5.

1.3.2 Impedance

$$Z(\omega) = \frac{1}{C i \omega} + \frac{L R i \omega}{R + L i \omega}$$

$$\operatorname{Re} Z(\omega) = \frac{L^2 R \omega^2}{L^2 \omega^2 + R^2}, \quad \operatorname{Im} Z(\omega) = \frac{L R^2 \omega}{L^2 \omega^2 + R^2} - \frac{1}{C \omega}$$

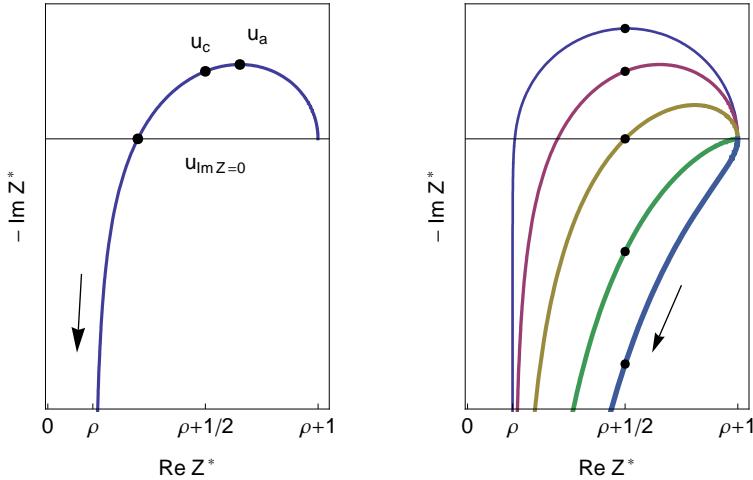


Figure 1.4: Nyquist diagram of the reduced impedance for the $(R_0 + (L + (R/C)))$ circuit (Fig. 1.1, Eq. (1.2)) plotted $\rho = 0.2$ and $T = 0.2$ (left) and $T = 0.01, 0.2, 0.5, 1, 1.5$ (right). The line thickness increases with increasing T . Dots: reduced characteristic angular frequency $u_c = 1$ (right).

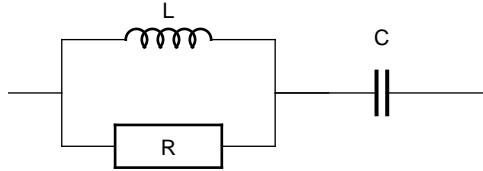


Figure 1.5: Circuit $(C + (R/L))$.

1.3.3 Reduced impedance

$$Z^*(u) = \frac{Z(u)}{R} = \frac{1}{iTu} + \frac{iu}{1+iu}, \quad u = \frac{L}{R}\omega, \quad T = \frac{R^2C}{L} \quad (1.3)$$

$$\text{Re } Z^*(u) = \frac{u^2}{u^2 + 1}, \quad \text{Im } Z^*(u) = \frac{u}{u^2 + 1} - \frac{1}{Tu}$$

Reduced characteristic angular frequency $u_c = 1$ with:

$$\text{Re } Z(u_c) = 1/2, \quad \text{Im } Z(u_c) = 1/2 - 1/T$$

$T > 1 \Rightarrow$:

- $u_{\text{Im } Z=0} = \frac{1}{\sqrt{T-1}}$, $\text{Re } Z(u_{\text{Im } Z=0}) = \frac{1}{T}$.

• reduced angular frequency at the apex :

$$u_a = \frac{1}{\sqrt{2}} \sqrt{\frac{T + \sqrt{T + 8\sqrt{T + 2}}}{T - 1}}$$

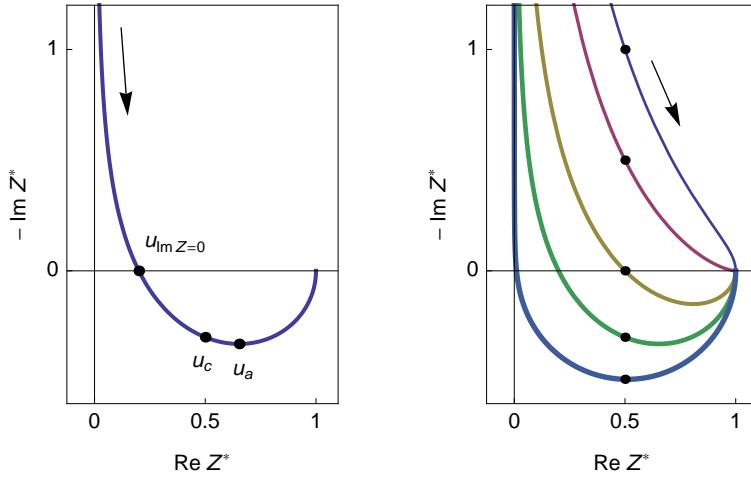


Figure 1.6: Nyquist diagram of the reduced impedance for the $(C+(R/L))$ circuit (Fig. 1.5, Eq. (1.3)) plotted for $T = 5$ (left) and $T = 0.66, 1, 2, 5, 100$ (right). The line thickness increases with increasing T . Dots: reduced characteristic angular frequency $u_c = 1$ (right).

with:

$$\begin{aligned} \operatorname{Re} Z(u_a) &= \frac{1}{4} \left(\frac{1}{\sqrt{\frac{T}{T+8}}} + 1 \right) \\ \operatorname{Im} Z(u_a) &= \frac{\sqrt{2}(T-1) (\sqrt{T} + \sqrt{T+8})}{T (3\sqrt{T} + \sqrt{T+8}) \sqrt{\frac{T+\sqrt{T+8}\sqrt{T+2}}{T-1}}} \end{aligned}$$

1.4 $(R/L)+(R/C)$ circuit

Fig. 1.7.

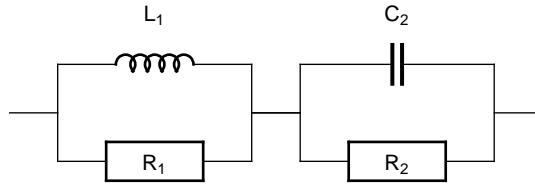


Figure 1.7: Circuit $(R/L)+(R/C)$.

1.4.1 Impedance

$$Z(\omega) = \frac{L_1 R_1 i \omega}{L_1 i \omega + R_1} + \frac{R_2}{C_2 R_2 i \omega + 1} = \frac{R_1 \tau_1 i \omega}{1 + \tau_1 i \omega} + \frac{R_2}{1 + \tau_2 i \omega}, \quad \tau_1 = \frac{L_1}{R_1}, \quad \tau_2 = R_2 C_2 \quad (1.4)$$

$$\begin{aligned}\operatorname{Re} Z(\omega) &= R_1 \left(1 - \frac{1}{\tau_1^2 \omega^2 + 1}\right) + \frac{R_2}{\tau_2^2 \omega^2 + 1}, \quad \operatorname{Im} Z(\omega) = \frac{R_1 \tau_1 \omega}{\tau_1^2 \omega^2 + 1} - \frac{R_2 \tau_2 \omega}{\tau_2^2 \omega^2 + 1} \\ \lim_{\omega \rightarrow 0} Z(\omega) &= R_2, \quad \lim_{\omega \rightarrow \infty} Z(\omega) = R_1\end{aligned}$$

1.4.2 Reduced impedance

$$\begin{aligned}Z^*(u) &= \frac{Z(\omega)}{R_2} = \rho \frac{i u}{1 + i u} + \frac{1}{1 + T i u}, \quad u = \omega \tau_1, \quad \rho = \frac{R_1}{R_2}, \quad T = \frac{\tau_2}{\tau_1} \\ \operatorname{Re} Z^*(u) &= \frac{u^2 \rho}{u^2 + 1} + \frac{1}{T^2 u^2 + 1}, \quad \operatorname{Im} Z^*(u) = \frac{u \rho}{u^2 + 1} - \frac{T u}{T^2 u^2 + 1}\end{aligned}$$

1.4.3 Nyquist impedance diagrams

- $T > 1$, Fig. 1.8.

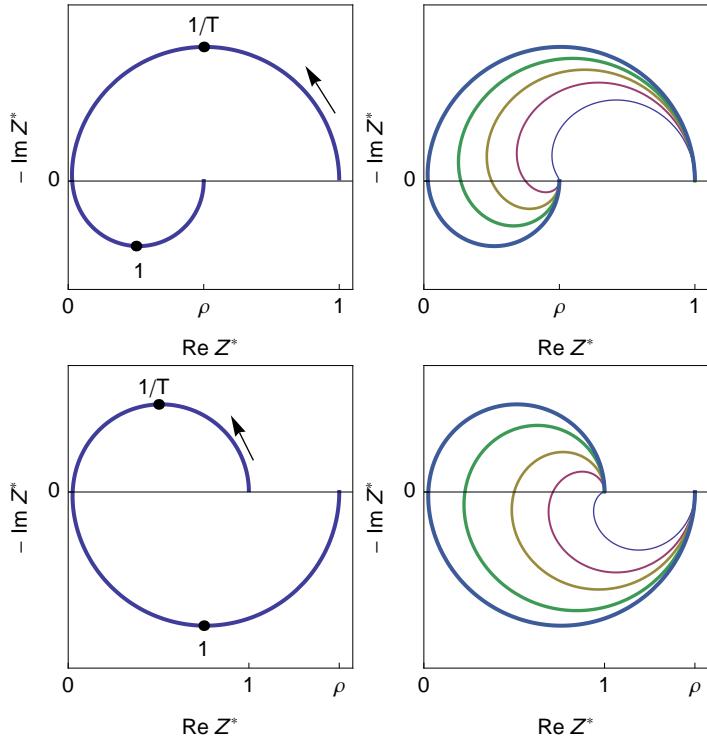


Figure 1.8: $T > 1$. Nyquist diagrams of the impedance for the $(R/L)+(R/C)$ circuit (Fig. 1.7, Eq. (1.4)) plotted for : top : $\rho < 1$ ($\rho = 0.5$), bottom : $\rho > 1$ ($\rho = 1.5$). $T \gg 1$ ($T = 10^2$) (left) and increasing values of T (right). The line thickness increases with increasing T .

- $T < 1$, Fig. 1.9.

- $T = 1$, Fig. 1.10.

$$T = 1 \Rightarrow Z^*(u) = \frac{1 + \rho i u}{1 + i u}$$

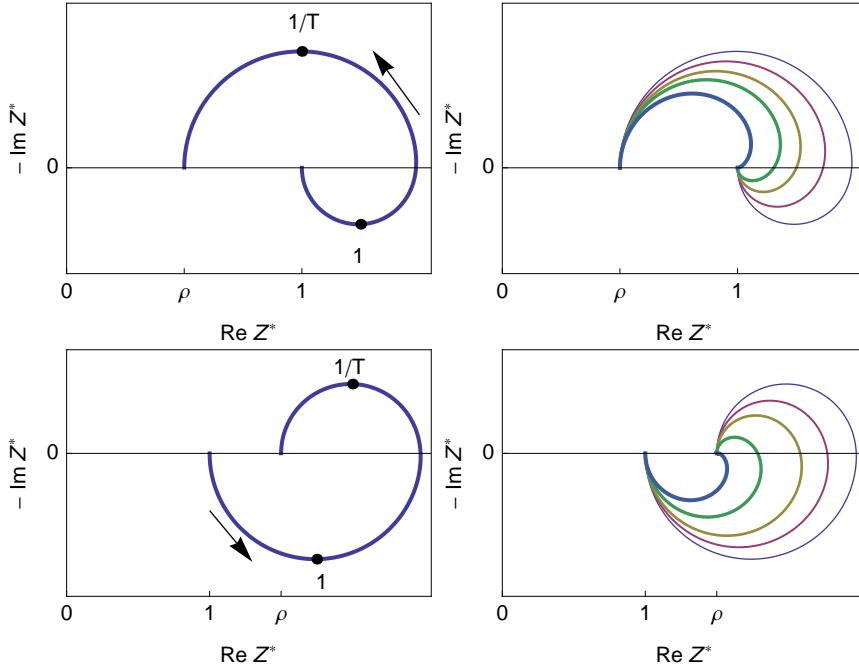


Figure 1.9: $T < 1$. Nyquist diagrams of the impedance for the $(R/L)+(R/C)$ circuit (Fig. 1.7, Eq. (1.4)) plotted for : top : $\rho < 1$ ($\rho = 0.5$), bottom : $\rho > 1$ ($\rho = 1.5$). $T \ll 1$ ($T = 10^{-2}$) (left) and increasing values of T (right). The line thickness increases with increasing T .

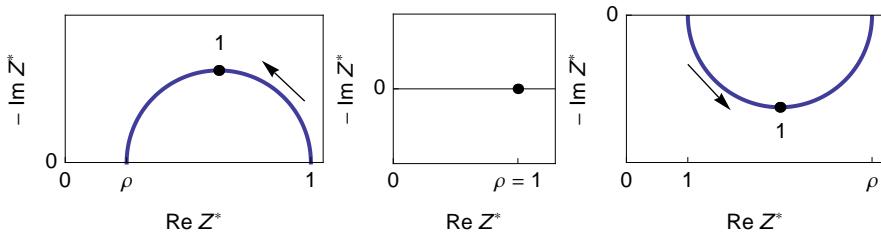


Figure 1.10: $T = 1$. Nyquist diagrams of the impedance for the $(R/L)+(R/C)$ circuit. Left: $\rho < 1$, middle: $\rho = 1$, right: $\rho > 1$.

1.4.4 Inductive and capacitive Nyquist diagrams

$$T > 1 \text{ and } \frac{1}{T} < \rho < T \text{ or } T < 1 \text{ and } T < \rho < \frac{1}{T}$$

$$\Rightarrow u_{\text{Im}=0} = \frac{\sqrt{T-\rho}}{\sqrt{T(T\rho-1)}}, \text{Re}_{\text{Im}=0} = \frac{1+\rho}{1+T}$$

Fig. 1.11.

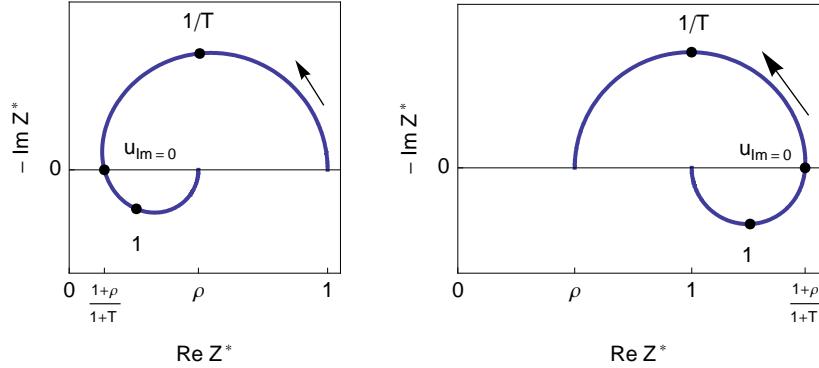


Figure 1.11: Inductive and capacitive Nyquist diagrams. Left : $T > 1$ and $\frac{1}{T} < \rho < T$, right : $T < 1$ and $T < \rho < \frac{1}{T}$.

1.4.5 $\rho = R_1/R_2 = 1$

$$Z^*(u) = \frac{i u}{1 + i u} + \frac{1}{1 + T i u}$$

Fig. 1.12.

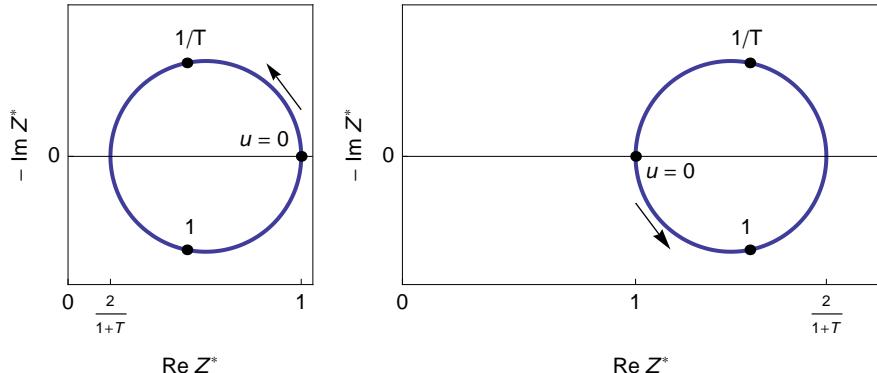


Figure 1.12: $\rho = R_1/R_2 = 1$. Nyquist diagram: full circle. Left: $T > 1$, right $T < 1$.

1.4.6 Array of Nyquist impedance diagrams

Fig. 1.13.

1.5 RLC parallel circuit

1.5.1 Circuit

Fig. 1.14.

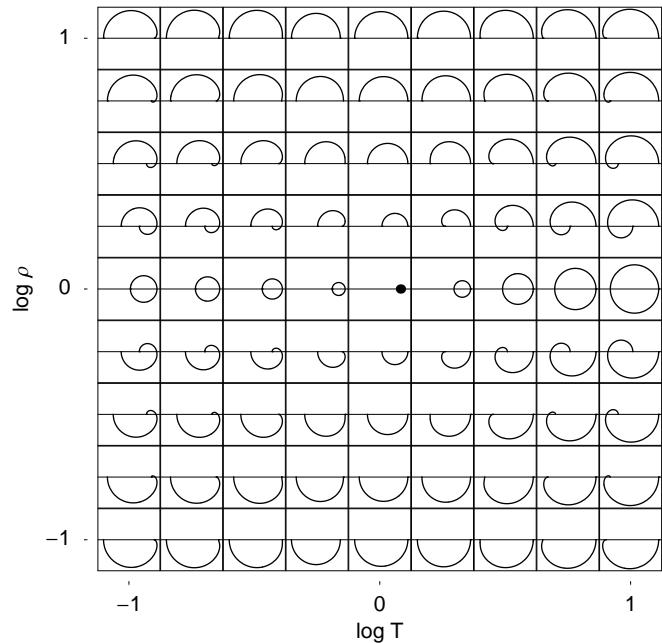


Figure 1.13: Array of Nyquist impedance diagrams for the $(R/L)+(R/C)$ circuit.
 $T = \rho = 1 \Rightarrow Z^*(u) = 1, \forall u.$

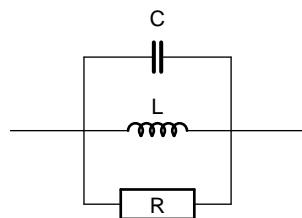


Figure 1.14: Circuit $((R/L)/C)$.

1.5.2 Admittance

$$Y(\omega) = \frac{1}{L i \omega} + C i \omega + \frac{1}{R} = \frac{L i \omega + R + C L R (i \omega)^2}{L R i \omega}$$

$$\operatorname{Re} Y(\omega) = \frac{1}{R}, \operatorname{Im} Y(\omega) = -\frac{1}{L \omega} + C \omega$$

$\operatorname{Re} Y(\omega)$ is constant, $\lim_{\omega \rightarrow 0} \operatorname{Im} Y(\omega) = -\infty, \lim_{\omega \rightarrow \infty} \operatorname{Im} Y(\omega) = \infty \Rightarrow$ Nyquist diagram of $Y(\omega)$ is a vertical straight line.

1.5.3 Reduced admittance

$$Y^*(u) = R Y(u) = 1 + \Lambda \left(i u + \frac{1}{i u} \right), \quad u = \omega \sqrt{LC}, \quad \Lambda = R \sqrt{\frac{C}{L}}$$

$$\operatorname{Re} Y^*(u) = 1, \quad \operatorname{Im} Y^*(u) = \Lambda \left(u - \frac{1}{u} \right)$$

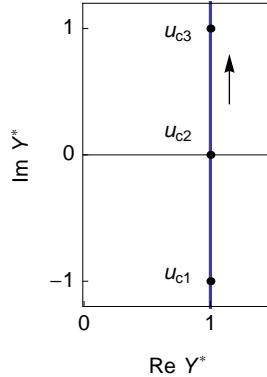


Figure 1.15: Nyquist diagram of the $((R/L)/C)$ circuit reduced admittance. $u_{c1} = (-1 + \sqrt{1 + 4\Lambda^2})/2\Lambda$, $u_{c2} = 1$, $u_{c3} = (1 + \sqrt{1 + 4\Lambda^2})/2\Lambda$.

1.5.4 Impedance

$$Z(\omega) = \frac{1}{Y(\omega)} = \frac{1}{\frac{1}{L i \omega} + C i \omega + \frac{1}{R}} = \frac{L R i \omega}{L i \omega + R + C L R (i \omega)^2}$$

$$\operatorname{Re} Z(\omega) = \frac{L^2 R \omega^2}{L^2 \omega^2 + (R - C L R \omega^2)^2}, \quad \operatorname{Im} Z(\omega) = \frac{L R^2 \omega (1 - C L \omega^2)}{L^2 \omega^2 + R^2 (-1 + C L \omega^2)^2}$$

The Nyquist diagram of $Y(\omega)$ is a vertical straight line \Rightarrow the Nyquist diagram of $Z(\omega)$ is a full circle.

1.5.5 Reduced impedance

$$Z^*(u) = \frac{Z(u)}{R} = \frac{i u}{\Lambda + i u + \Lambda (i u)^2}, \quad u = \omega \sqrt{LC}, \quad \Lambda = R \sqrt{\frac{C}{L}}$$

$$\operatorname{Re} Z^*(u) = \frac{u^2}{u^2 + \Lambda^2 (1 - u^2)^2}, \quad \operatorname{Im} Z^*(u) = \frac{\Lambda u (1 - u^2)}{u^2 + \Lambda^2 (1 - u^2)^2}$$

1.6 RLC serie circuit

1.6.1 Circuit

Fig. 1.17.

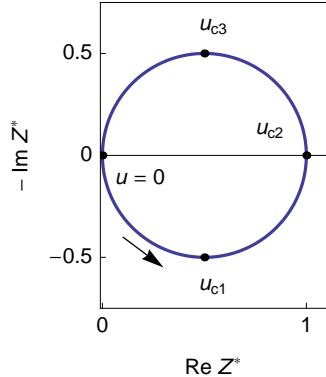


Figure 1.16: Nyquist diagram of the $((R/L)/C)$ circuit reduced impedance. $u_{c1} = (-1 + \sqrt{1 + 4\Lambda^2})/2\Lambda$, $u_{c2} = u_r = 1$, $u_{c3} = (1 + \sqrt{1 + 4\Lambda^2})/2\Lambda$ ($u_{c3} - u_{c1} = \Lambda$).

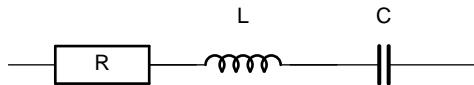


Figure 1.17: Circuit $((R+L)+C)$.

1.6.2 Impedance

$$Z(\omega) = R + L i \omega + \frac{1}{C i \omega} = \frac{1 + R C i \omega + C L (i \omega)^2}{C i \omega}$$

$$\text{Re } Z(\omega) = R, \text{Im } Z(\omega) = -\frac{1}{C \omega} + L \omega$$

$\text{Re } Z(\omega)$ is constant, $\lim_{\omega \rightarrow 0} \text{Im } Z(\omega) = -\infty$, $\lim_{\omega \rightarrow \infty} \text{Im } Z(\omega) = \infty \Rightarrow$ Nyquist diagram of $Z(\omega)$ is a vertical straight line.

1.6.3 Reduced impedance

$$Z^*(u) = \frac{Z(u)}{R} = 1 + \frac{1}{\Lambda} \left(i u + \frac{1}{i u} \right), \quad u = \omega \sqrt{LC}, \quad \Lambda = R \sqrt{\frac{C}{L}}$$

$$\text{Re } Z^*(u) = 1, \quad \text{Im } Z^*(u) = \frac{1}{\Lambda} \left(u - \frac{1}{u} \right)$$

1.6.4 Admittance

$$Y(\omega) = \frac{1}{Z(\omega)} = \frac{C i \omega}{1 + R C i \omega + C L (i \omega)^2}$$

$$\text{Re } Y(\omega) = -\frac{C^2 R \omega^2}{C^2 R^2 \omega^2 + (-1 + C L \omega^2)^2}, \quad \text{Im } Y(\omega) = \frac{C \omega (1 - C L \omega^2)}{1 + C \omega^2 (C R^2 + L (-2 + C L \omega^2))}$$

The Nyquist diagram of $Z(\omega)$ is a vertical straight line \Rightarrow the Nyquist diagram of $Y(\omega)$ is a full circle.

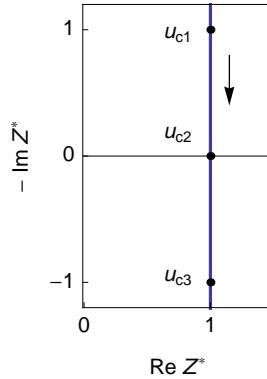


Figure 1.18: Nyquist diagram of the $((R+L)+C)$ circuit reduced impedance. $u_{c1} = (-\Lambda + \sqrt{4 + \Lambda^2})/2$, $u_{c2} = 1$, $u_{c3} = (\Lambda + \sqrt{4 + \Lambda^2})/2$.

1.6.5 Reduced admittance

$$Y^*(u) = R Y(u) = \frac{\Lambda i u}{1 + \Lambda i u + (i u)^2}, \quad u = \omega \sqrt{LC}, \quad \Lambda = R \sqrt{\frac{C}{L}}$$

$$\text{Re } Y^*(u) = \frac{u^2 \Lambda^2}{1 + u^4 + u^2 (-2 + \Lambda^2)}, \quad \text{Im } Y^*(u) = \frac{u \Lambda (1 - u^2)}{1 + u^4 + u^2 (-2 + \Lambda^2)}$$

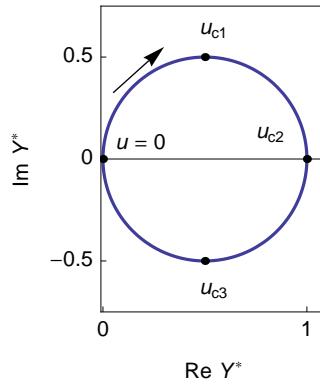


Figure 1.19: Nyquist diagram of the $((R+L)+C)$ circuit reduced admittance. $u_{c1} = (-\Lambda + \sqrt{4 + \Lambda^2})/2$, $u_{c2} = u_r = 1$, $u_{c3} = (\Lambda + \sqrt{4 + \Lambda^2})/2$, $(u_{c3} - u_{c1} = \Lambda)$.


1.7 $R_0 + RLC$ parallel circuit

1.7.1 Circuit


Fig. 1.20.

1.7.2 Impedance

$$Z(\omega) = R_0 + \frac{L R i \omega}{L i \omega + R + C L R (i \omega)^2} \quad (1.5)$$

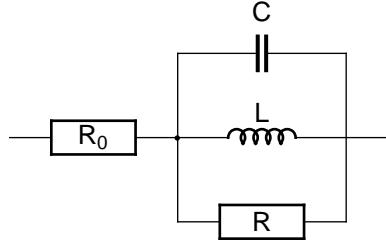
 Figure 1.20: $R_0 + \text{RLC}$ parallel circuit.

$$Z^*(u) = \frac{Z(u)}{R} = \rho + \frac{i u}{\Lambda + i u + \Lambda (i u)^2}, \quad \rho = \frac{R_0}{R}, \quad u = \omega \sqrt{L C}, \quad \Lambda = R \sqrt{\frac{C}{L}}$$

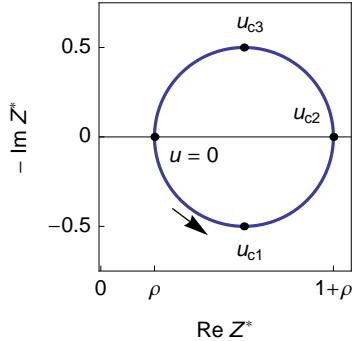
 Figure 1.21: Nyquist reduced impedance diagram of the $R_0 + \text{RLC}$ parallel circuit.
 $u_{c1} = (-1 + \sqrt{1 + 4 \Lambda^2})/2 \Lambda, \quad u_{c2} = u_r = 1, \quad u_{c3} = (1 + \sqrt{1 + 4 \Lambda^2})/2 \Lambda \quad (u_{c3} - u_{c1} = \Lambda).$

1.8 Transformation formulae $(R_1/L_1)+(R_1/C_2) \rightarrow r_1 + \text{RLC parallel}$

$r_1 + r_2/l_2/c_2$ parallel circuit is not-distinguishable from $(R_1/L_1)+(R_1/C_2)$ circuit for $R_1^2 C_2 / L_2 > 1$ (Fig. 1.22).

$$Z(p) = \frac{R_1 \left(C_2 L_1 p^2 + \frac{2 L_1 p}{R_1} + 1 \right)}{C_2 L_1 p^2 + \frac{p(C_2 R_1^2 + L_1)}{R_1} + 1} \quad (1.6)$$

$$z(p) = \frac{r_1 \left(c_2 l_2 p^2 + \frac{l_2 p(r_1 + r_2)}{r_1 r_2} + 1 \right)}{c_2 l_2 p^2 + \frac{l_2 p}{r_2} + 1} \quad (1.7)$$

$$c_2 = \frac{C_2 L_1}{L_1 - C_2 R_1^2}, \quad l_2 = L_1 - C_2 R_1^2, \quad r_2 = R_1 \left(\frac{2 L_1}{C_2 R_1^2 + L_1} - 1 \right) \quad (1.8)$$

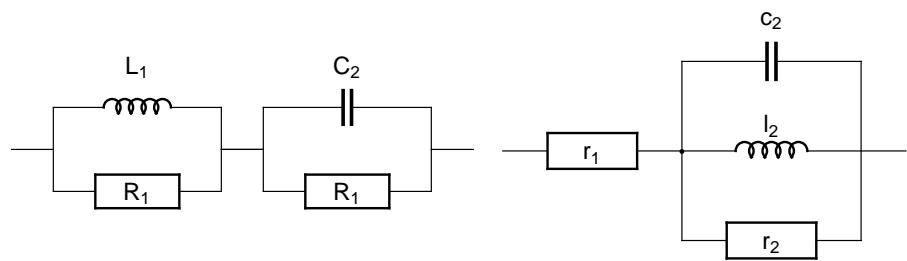


Figure 1.22: $(R_1/L_1)+(R_1/C_2)$ ($(R_1/L_1)+(R_2/C_2)$ circuit with $R_1 = R_2$) and $r_1+r_2/l_2/c_2$ parallel circuit.

Chapter 2

Quartz resonator

2.1 BVD equivalent circuit

Fig. 2.1, [3, 5, 6, 1].

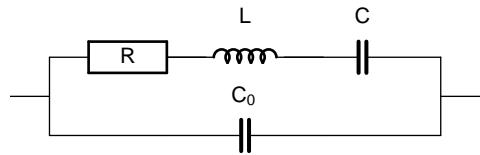


Figure 2.1: BVD (Butterworth-van Dyke)-equivalent circuit of a quartz resonator.

2.2 Admittance



$$Y(\omega) = \frac{1}{R + L i \omega + \frac{1}{C i \omega}} + i \omega C_0 = i \omega \left(\frac{C}{1 + C i \omega (L i \omega + R)} + C_0 \right)$$

$$\operatorname{Re} Y(\omega) = \frac{C^2 R \omega^2}{C^2 R^2 \omega^2 + (-1 + C L \omega^2)^2}, \quad \operatorname{Im} Y(\omega) = \omega \left(\frac{C (1 - C L \omega^2)}{1 + C \omega^2 (C R^2 + L (-2 + C L \omega^2))} + C_0 \right)$$

2.3 Reduced admittance

$$Y^*(u) = R Y(u) = \frac{\Lambda i u}{1 + \Lambda i u + (i u)^2} + \gamma i u, \quad u = \omega \sqrt{LC}, \quad \Lambda = R \sqrt{\frac{C}{L}}, \quad \gamma = \frac{R C_0}{\sqrt{LC}}$$

$$\operatorname{Re} Y^*(u) = \frac{u^2 \Lambda^2}{1 + u^4 + u^2 (-2 + \Lambda^2)}, \quad \operatorname{Im} Y^*(u) = u \gamma + \frac{u \Lambda (1 - u^2)}{1 + u^4 + u^2 (-2 + \Lambda^2)}$$

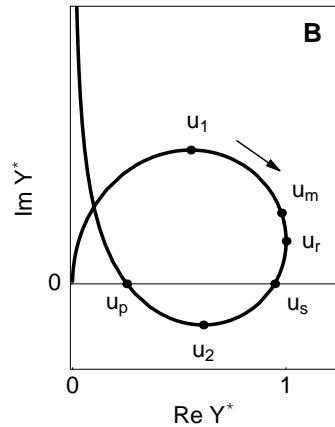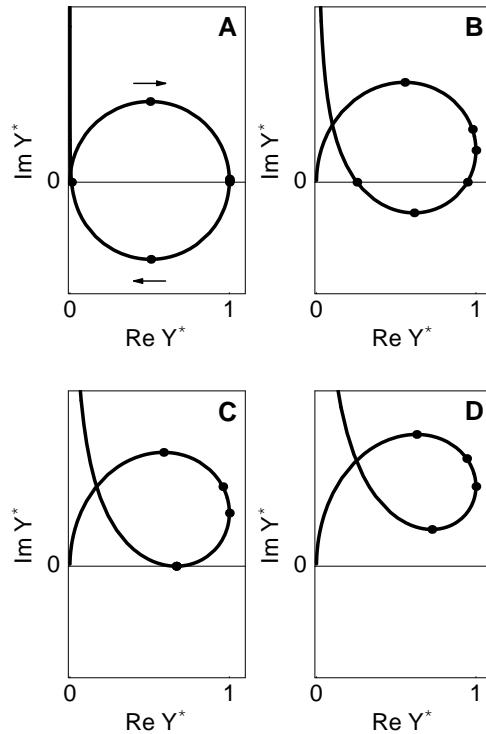Figure 2.2: Definitions for u_1 , u_m , u_r , u_s , u_2 and u_p .Figure 2.3: Change of admittance diagram with γ . $\Lambda = 1$, $\gamma = 10^{-2}$ (A), 2×10^{-1} (B), $1/3$ (C), $1/2$ (D).

2.3.1 Characteristic frequencies

- Maximum of the real part of Y^* for:
 $u_r = 1 \Rightarrow \text{Re } Y^*(u_r) = 1, \text{Im } Y^*(u_r) = \gamma$

- Zero-phase reduced angular frequencies: u_s and u_p defined for $\gamma < 1/(2 + \Lambda)$:

$$1. \quad \gamma < \frac{1}{2 + \Lambda} \Rightarrow$$

$$u_s = \sqrt{\frac{\Lambda - \gamma (-2 + \Lambda^2) - \Lambda \sqrt{1 - 2\gamma\Lambda + \gamma^2 (-4 + \Lambda^2)}}{2\gamma}},$$

$$\operatorname{Re} Y^*(u_s) = \frac{1}{2} \left(1 + \gamma\Lambda + \sqrt{(\gamma(\Lambda - 2) - 1)(\gamma(\Lambda + 2) - 1)} \right)$$

$$u_p = \sqrt{\frac{2\gamma + \Lambda - \gamma\Lambda^2 + \Lambda \sqrt{1 - 2\gamma\Lambda + \gamma^2 (-4 + \Lambda^2)}}{2\gamma}},$$

$$\operatorname{Re} Y^*(u_p) = \frac{1}{2} \left(1 + \gamma\Lambda - \sqrt{(\gamma(\Lambda - 2) - 1)(\gamma(\Lambda + 2) - 1)} \right)$$

$$2. \quad \gamma = \frac{1}{2 + \Lambda} \Rightarrow$$

$$u_s = u_p = \frac{-\gamma\Lambda^2 + 2\gamma + \Lambda}{2\gamma}$$

$$\operatorname{Re} Y^*(u_s) = \operatorname{Re} Y^*(u_p) = \frac{1}{2}(1 + \gamma\Lambda) \quad (\text{Fig. 2.3C}).$$

$$3. \quad \gamma > \frac{1}{2 + \Lambda} \Rightarrow$$

no zero-phase reduced angular frequency (Fig. 2.3D).

Real quartz : $C_0 \approx 10^{-12}$ F, $C \approx 10^{-14}$ F, $R \approx 100$ Ω, $L \approx \times 10^{-2}$ H $\Rightarrow \Lambda \approx 10^{-4}$ and $\gamma \approx 10^{-2}$ [4, 2].

Bibliography

- [1] ARNAU, A., SOGORB, T., AND JIMÉNEZ, Y. A continuous motional series resonant frequency monitoring circuit and a new method of determining Butterworth-Van Dyke parameters of a quartz crystal microbalance in fluid media. *Rev. Sci. Instrum.* 71 (2000), 2563–2571.
- [2] BIZET, K., GABRIELLI, C., PERROT, H., AND TERRASSE, J. Validation of antibody-based recognition by piezoelectric transducers through electroacoustic admittance analysis. *Biosensors & Bioelectronics* 13 (1998), 259–269.
- [3] BUTTERWORTH, S. *Proc. Phys. Soc. London* 27 (1915), 410.
- [4] BUTTRY, D. A., AND WARD, M. D. Measurement of interfacial processes at electrode surfaces with the electrochemical quartz crystal microbalance. *Chem. Rev.* 92 (1992), 1355–1379.
- [5] VANDYKE, K. S. *Phys. Rev* 25 (1925), 895.
- [6] VANDYKE, K. S. In *Proceeding of the 1928 IEEE International Frequency Control Symposium* (New York, 1928), vol. 16, IEEE, p. 742.