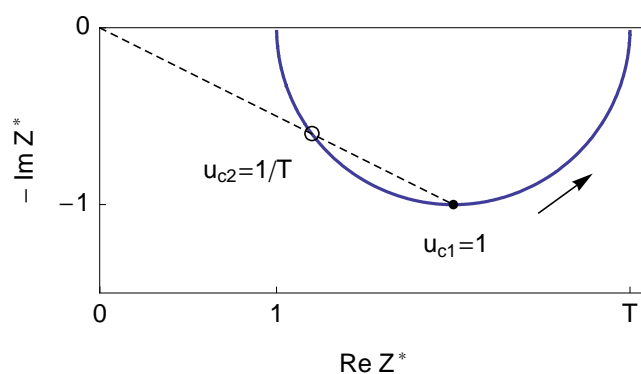


Handbook of Electrochemical Impedance Spectroscopy



CIRCUITS made of RESISTORS and INDUCTORS

ER@SE/LEPMI
J.-P. Diard, B. Le Gorrec, C. Montella

Hosted by Bio-Logic @ www.bio-logic.info



September 6, 2007

Contents

1	Circuits containing one L	5
1.1	Circuit $(R+L)$	5
1.1.1	Impedance	5
1.1.2	Reduced impedance	5
1.2	Circuit (R/L)	6
1.2.1	Impedance	6
1.2.2	Reduced impedance	6
1.3	Circuit $(R_2+(R_1/L_1))$	7
1.3.1	Impedance	7
1.3.2	Reduced impedance	7
1.4	Circuit $((R_1+L_1)/R_2)$	8
1.4.1	Impedance	8
1.4.2	Reduced impedance	8
1.5	Transformation formulae	
	$(R+(R/L)) \leftrightarrow ((R+L)/R)$	8
1.5.1	Transformation formulae $(R+(R/L)) \rightarrow ((R+L)/R)$. . .	8
1.5.2	Transformation formulae $((R+L)/R) \rightarrow (R+(R/L))$. . .	9
1.6	Circuits containing L vs. circuits containing C	9
1.6.1	Transformation formulae circuit 1 \leftrightarrow circuit 2 and circuit 3 \leftrightarrow circuit 4	9
1.6.2	Transformation formulae circuit 3 \rightarrow circuit 1	9
1.6.3	Transformation formulae circuit 1 \rightarrow circuit 3	9
1.6.4	Transformation formulae circuit 4 \rightarrow circuit 1	9
1.6.5	Transformation formulae circuit 1 \rightarrow circuit 4	10
1.6.6	Transformation formulae circuit 3 \rightarrow circuit 2	10
1.6.7	Transformation formulae circuit 2 \rightarrow circuit 3	10
1.6.8	Transformation formulae circuit 4 \rightarrow circuit 2	10
1.6.9	Transformation formulae circuit 2 \rightarrow circuit 4	10
1.7	Modified inductance	10
2	Circuits made of one R and two Ls	11
2.1	Circuit $((R_1/L_1)+L_2)$	11
2.1.1	Impedance	11
2.1.2	Time constants	11
2.1.3	Reduced impedance	12
2.2	Circuit $((R_1+L_2)/L_1)$	12
2.2.1	Impedance	13

2.2.2	Time constants	13
2.2.3	Reduced impedance	13
2.3	Transformation formulae $((R/L)+L) \leftrightarrow ((R+L)/L)$	13
2.3.1	Transformation formulae $((R/L)+L) \rightarrow ((R+L)/L)$	13
2.3.2	Transformation formulae $((R+L)/L) \rightarrow ((R/L)+L)$	13

Chapter 1

Circuits containing one L

1.1 Circuit (R+L)

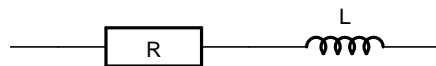


Figure 1.1: Circuit (R+L).

1.1.1 Impedance

$$Z(\omega) = R + iL\omega, \text{Re } Z(\omega) = R, \text{Im } Z(\omega) = L\omega$$

1.1.2 Reduced impedance

$$Z^*(u) = Z/R = 1 + iu, u = \omega\tau, \tau = L/R$$

$$\text{Re } Z^*(u) = 1, \text{Im } Z^*(u) = u$$

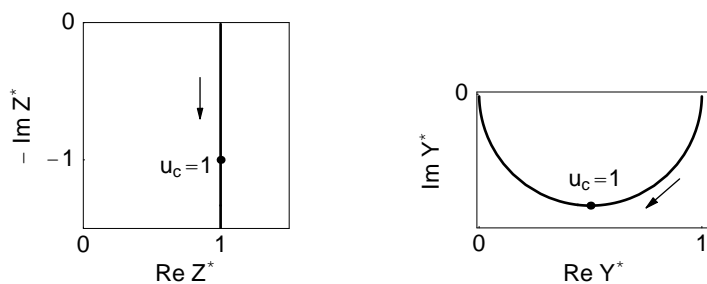


Figure 1.2: Nyquist diagrams of reduced impedance and admittance ($Y^* = RY$) for the (R+L) circuit.

1.2 Circuit (R/L)

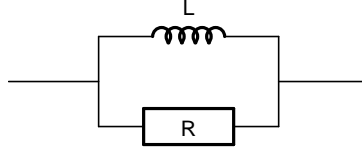


Figure 1.3: Circuit (R/L).

1.2.1 Impedance


$$Z(\omega) = \frac{1}{\frac{1}{i\omega L} + \frac{1}{R}} = \frac{iLR\omega}{R + iL\omega}$$

$$\operatorname{Re} Z(\omega) = \frac{L^2 R \omega^2}{R^2 + L^2 \omega^2}, \quad \operatorname{Im} Z(\omega) = \frac{LR^2 \omega}{R^2 + L^2 \omega^2}$$


1.2.2 Reduced impedance

$$Z^*(u) = \frac{Z}{R} = \frac{i u}{1 + i u}, \quad u = \omega \tau, \quad \tau = L/R$$

$$\operatorname{Re} Z^*(u) = \frac{u^2}{1 + u^2}, \quad \operatorname{Im} Z^*(u) = \frac{u}{1 + u^2}$$

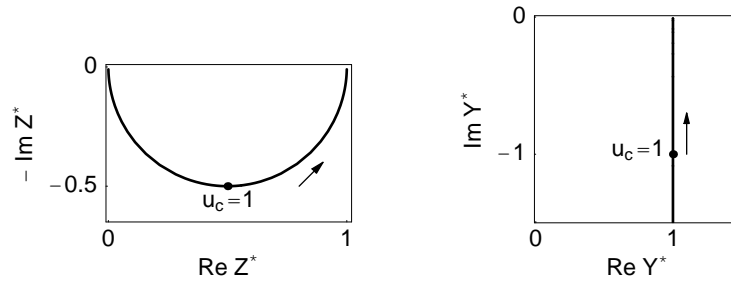Figure 1.4: Nyquist diagrams of reduced impedance and admittance ($Y^* = RY$) for the (R/L) circuit.

1.3 Circuit ($R_2+(R_1/L_1)$)

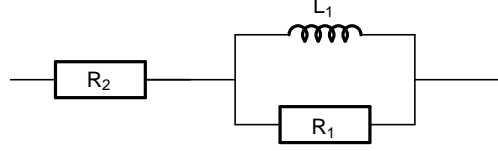Figure 1.5: Circuit ($R_2+(R_1/L_1)$).

1.3.1 Impedance

$$Z(\omega) = R_2 + \frac{1}{\frac{1}{i\omega L_1} + \frac{1}{R_1}} = \frac{R_2 \left(1 + \frac{i\omega L_1 (R_1 + R_2)}{R_1 R_2} \right)}{1 + \frac{i\omega L_1}{R_1}}$$

$$\operatorname{Re} Z(\omega) = \frac{\omega^2 L_1^2 R_1}{\omega^2 L_1^2 + R_1^2} + R_2, \quad \operatorname{Im} Z(\omega) = \frac{\omega L_1 R_1^2}{\omega^2 L_1^2 + R_1^2}$$


1.3.2 Reduced impedance

$$Z^*(u) = Z/R_2 = \frac{1 + iTu}{1 + iu}, \quad u = \tau_1 \omega, \quad \tau_1 = L_1/R_1 \quad (1.1)$$


$$T = (R_1 + R_2)/R_2 = 1 + R_1/R_2 > 1$$

$$\operatorname{Re} Z^*(u) = \frac{1 + Tu^2}{1 + u^2}, \quad \operatorname{Im} Z^*(u) = \frac{(-1 + T)u}{1 + u^2}$$

$$\lim_{u \rightarrow 0} \operatorname{Re} Z^*(u) = 1, \quad \lim_{u \rightarrow \infty} \operatorname{Re} Z^*(u) = T$$

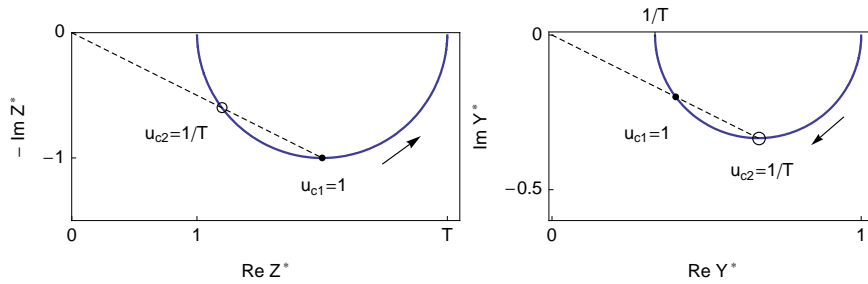Figure 1.6: Nyquist diagram of reduced impedance and admittance ($Y^* = R_2 Y$) for the ($R_2+(R_1/L_1)$) circuit, plotted for $T = 3$.

1.4 Circuit $((R_1+L_1)/R_2)$

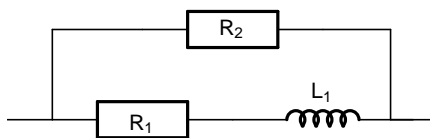Figure 1.7: Circuit $((R_1+L_1)/R_2)$.

1.4.1 Impedance

$$Z(\omega) = \frac{(i\omega L_1 + R_1) R_2}{i\omega L_1 + R_1 + R_2} = \frac{R_1 R_2 \left(1 + \frac{i\omega L_1}{R_1}\right)}{(R_1 + R_2) \left(1 + \frac{i\omega L_1}{R_1 + R_2}\right)}$$

$$\operatorname{Re} Z(\omega) = \frac{R_2 (\omega^2 L_1^2 + R_1 (R_1 + R_2))}{\omega^2 L_1^2 + (R_1 + R_2)^2}, \quad \operatorname{Im} Z(\omega) = \frac{\omega L_1 R_2^2}{\omega^2 L_1^2 + (R_1 + R_2)^2}$$

1.4.2 Reduced impedance

$$Z^*(u) = \frac{Z(R_1 + R_2)}{R_1 R_2} = \frac{1 + iTu}{1 + iu}, \quad u = \tau_1 \omega, \quad \tau_1 = L_1 / (R_1 + R_2)$$

$$T = \tau_2 / \tau_1, \quad \tau_2 = L_1 / R_1, \quad T = 1 + R_2 / R_1 > 1$$

cf. § 1.3.2, Eq. (1.1) and Fig. 1.6.

1.5 Transformation formulae $(R+(R/L)) \leftrightarrow ((R+L)/R)$

Figure 1.8: The $(R+(R/L))$ and $((R+L)/R)$ circuits are non-distinguishable.

1.5.1 Transformation formulae $(R+(R/L)) \rightarrow ((R+L)/R)$

$$R_{22} = R_{11} + R_{21}, \quad L_{12} = \frac{L_{11}}{R_{11}}, \quad R_{12} = R_{21} + \frac{R_{21}^2}{R_{11}}$$

1.5.2 Transformation formulae $((\mathbf{R}+\mathbf{L})/\mathbf{R}) \rightarrow (\mathbf{R}+(\mathbf{R}/\mathbf{L}))$

$$L_{11} = \frac{L_{12} R_{22}^2}{R_{12} + R_{22}}, R_{11} = \frac{R_{22}^2}{R_{12} + R_{22}}, R_{21} = \frac{R_{12} R_{22}}{R_{12} + R_{22}}$$

1.6 Circuits containing L vs. circuits containing C

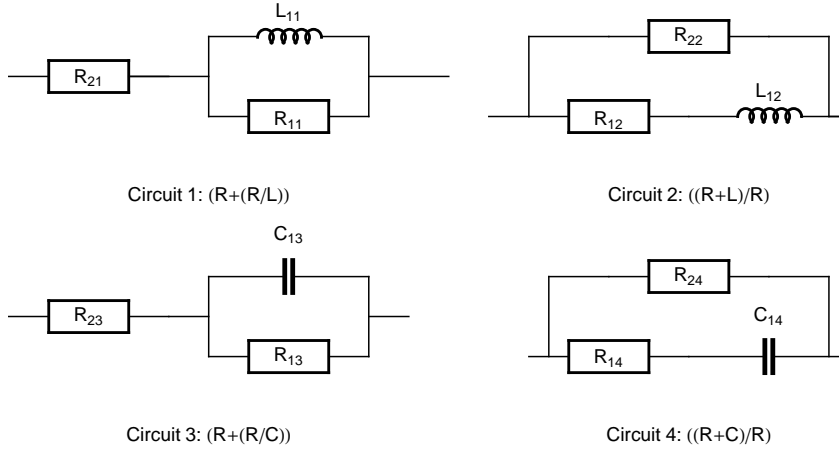


Figure 1.9: $(\mathbf{R}+(\mathbf{R}/\mathbf{L}))$, $((\mathbf{R}+\mathbf{L})/\mathbf{R})$, $(\mathbf{R}+(\mathbf{R}/\mathbf{C}))$, $((\mathbf{R}+\mathbf{C})/\mathbf{R})$ circuits are non-distinguishable, taking account of negative values of parameters.

1.6.1 Transformation formulae circuit 1 \leftrightarrow circuit 2 and circuit 3 \leftrightarrow circuit 4

cf. § 1.5 and "Handbook of EIS : Circuits made of Rs and Cs".

1.6.2 Transformation formulae circuit 3 \rightarrow circuit 1

$$L_{11} = -C_{13} R_{13}^2, R_{21} = R_{13} + R_{23}, R_{11} = -R_{13}$$

1.6.3 Transformation formulae circuit 1 \rightarrow circuit 3

$$C_{13} = -\frac{L_{11}}{R_{11}^2}, R_{23} = R_{11} + R_{21}, R_{13} = -R_{11}$$

1.6.4 Transformation formulae circuit 4 \rightarrow circuit 1

$$L_{11} = -C_{14} R_{24}^2, R_{21} = R_{24}, R_{11} = -\frac{R_{24}^2}{R_{14} + R_{24}}$$

1.6.5 Transformation formulae circuit 1 \rightarrow circuit 4

$$R_{24} = R_{21}, R_{14} = -\frac{R_{21} (R_{11} + R_{21})}{R_{11}}, C_{14} = -\frac{L_{11}}{R_{21}^2}$$

1.6.6 Transformation formulae circuit 3 \rightarrow circuit 2

$$L_{12} = C_{13} R_{13}, R_{22} = R_{23}, R_{12} = -\frac{R_{23} (R_{13} + R_{23})}{R_{13}}$$

1.6.7 Transformation formulae circuit 2 \rightarrow circuit 3

$$C_{13} = -\frac{L_{12} (R_{12} + R_{22})}{R_{22}^2}, R_{23} = R_{22}, R_{13} = -\frac{R_{22}^2}{R_{12} + R_{22}}$$

1.6.8 Transformation formulae circuit 4 \rightarrow circuit 2

$$L_{12} = C_{14} (R_{14} + R_{24}), R_{22} = \frac{R_{14} R_{24}}{R_{14} + R_{24}}, R_{12} = -R_{14}$$

1.6.9 Transformation formulae circuit 2 \rightarrow circuit 4

$$R_{14} = -R_{12}, R_{24} = \frac{R_{12} R_{22}}{R_{12} + R_{22}}, C_{14} = -\frac{L_{12} (R_{12} + R_{22})}{R_{12}^2}$$

1.7 Modified inductance

$$Z = L_\alpha (i\omega)^\alpha, \operatorname{Re} Z = L_\alpha \omega^\alpha c_\alpha, \operatorname{Im} Z = L_\alpha \omega^\alpha s_\alpha$$

$$c_\alpha = \cos\left(\frac{\pi \alpha}{2}\right), s_\alpha = \sin\left(\frac{\pi \alpha}{2}\right)$$

$$|Z| = L_\alpha \omega^\alpha, \phi_Z = \frac{\pi \alpha}{2} = \text{cte}$$

The L_α unit ($\text{H cm}^2 \text{s}^{1-\alpha}$) depends on α .

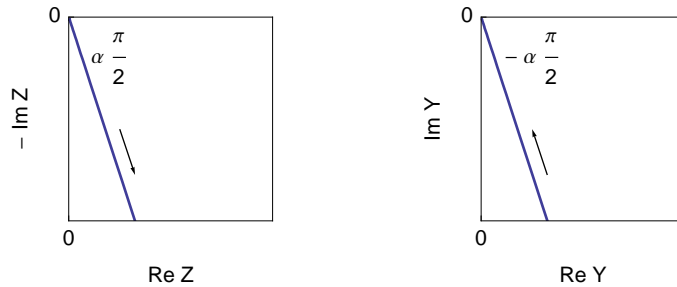


Figure 1.10: Nyquist diagrams of the impedance and admittance for the modified inductance L_α , plotted for $\alpha = 0.8$.

Chapter 2

Circuits made of one R and two Ls

2.1 Circuit $((R_1/L_1)+L_2)$

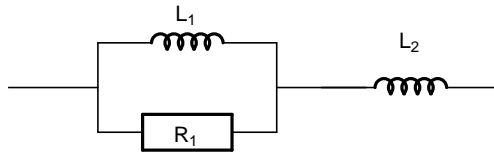


Figure 2.1: Circuit $((R_1/L_1)+L_2)$.

2.1.1 Impedance

$$Z(\omega) = \frac{1}{\frac{1}{R_1} + \frac{1}{i\omega L_1}} + i\omega L_2 = \frac{i\omega (L_1 + L_2) \left(1 + \frac{i\omega L_1 L_2}{(L_1 + L_2) R_1}\right)}{1 + \frac{i\omega L_1}{R_1}}$$

2.1.2 Time constants

$$Z(\omega) = \frac{(L_1 + L_2) i\omega (1 + i\omega \tau_2)}{1 + i\omega \tau_1}, \quad \tau_1 = \frac{L_1}{R_1}, \quad \tau_2 = \frac{L_1 L_2}{(L_1 + L_2) R_1}$$

$$\operatorname{Re} Z(\omega) = \frac{\omega^2 (L_1 + L_2) (\tau_1 - \tau_2)}{1 + \omega^2 \tau_1^2}, \quad \operatorname{Im} Z(\omega) = \frac{\omega (L_1 + L_2) (1 + \omega^2 \tau_1 \tau_2)}{1 + \omega^2 \tau_1^2}$$

$$\lim_{\omega \rightarrow \infty} \operatorname{Re} Z(\omega) = \frac{(L_1 + L_2) (\tau_1 - \tau_2)}{\tau_1^2} = R_1$$

2.1.3 Reduced impedance

$$Z^*(u) = Z(\omega)/R_1 = \frac{1}{1-T} \frac{i u (1+i T u)}{1+i u} \quad (2.1)$$

$$u = \omega \tau_1, \quad T = \frac{\tau_2}{\tau_1} = \frac{L_2}{L_1 + L_2} < 1$$

$$\operatorname{Re} Z^*(u) = \frac{u^2}{1+u^2}, \quad \operatorname{Im} Z^*(u) = -\frac{u(1+T u^2)}{(-1+T)(1+u^2)}, \quad \lim_{u \rightarrow \infty} \operatorname{Re} Z(u) = 1$$

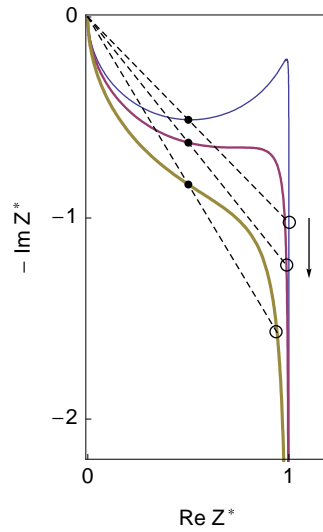


Figure 2.2: Nyquist diagrams of reduced impedance for the $((R_1/L_1)+L_2)$ circuit (Eq. (2.1), Fig. 2.1, $T = 1/4, 1/9, 1/90$, the line thickness increases with increasing T). Horizontal tangent for $T \leq 1/9$ ($L_1/L_2 \geq 8$). Dots: reduced characteristic frequency: $u_{c1} = 1$; circles: reduced characteristic angular frequency $u_{c2} = 1/T$.

2.2 Circuit $((R_1+L_2)/L_1)$

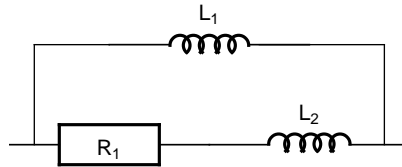


Figure 2.3: Circuit $((R_1+L_2)/L_1)$.

2.2.1 Impedance

$$Z(\omega) = \frac{i\omega L_1 (i\omega L_2 + R_1)}{i\omega L_1 + i\omega L_2 + R_1} = \frac{i\omega L_1 \left(1 + \frac{i\omega L_2}{R_1}\right)}{1 + \frac{i\omega (L_1 + L_2)}{R_1}}$$

2.2.2 Time constants

$$Z(\omega) = \frac{i\omega L_1 (1 + i\omega \tau_2)}{1 + i\omega \tau_1}, \quad \tau_1 = \frac{L_1 + L_2}{R_1}, \quad \tau_2 = \frac{L_2}{R_1}$$

$$\operatorname{Re} Z(\omega) = \frac{\omega^2 L_1 (\tau_1 - \tau_2)}{1 + \omega^2 \tau_1^2}, \quad \operatorname{Im} Z(\omega) = \frac{\omega L_1 (1 + \omega^2 \tau_1 \tau_2)}{1 + \omega^2 \tau_1^2}$$

$$\lim_{\omega \rightarrow \infty} \operatorname{Re} Z(\omega) = \frac{L_1 (\tau_1 - \tau_2)}{\tau_1^2} = \frac{L_1^2 R_1}{(L_1 + L_2)^2}$$

2.2.3 Reduced impedance

$$Z^*(u) = Z(\omega)/R_1 = (1 - T) \frac{i u (1 + iTu)}{1 + iu} \quad (2.2)$$

$$u = \omega \tau_1, \quad T = \frac{\tau_2}{\tau_1} = \frac{L_2}{L_1 + L_2} < 1$$

$$\operatorname{Re} Z^*(u) = \frac{(-1 + T)^2 u^2}{1 + u^2}, \quad \operatorname{Im} Z^*(u) = -\frac{(-1 + T) u (1 + Tu^2)}{1 + u^2}$$

$$\lim_{u \rightarrow \infty} \operatorname{Re} Z^*(u) = \frac{L_1^2}{(L_1 + L_2)^2}$$

(Fig. 2.4)

2.3 Transformation formulae $((R/L)+L) \leftrightarrow ((R+L)/L)$

2.3.1 Transformation formulae $((R/L)+L) \rightarrow ((R+L)/L)$

$$R_{12} = \frac{(L_{11} + L_{21})^2 R_{11}}{L_{11}^2}, \quad L_{22} = L_{21} + \frac{L_{21}^2}{L_{11}}, \quad L_{12} = L_{11} + L_{21}$$

2.3.2 Transformation formulae $((R+L)/L) \rightarrow ((R/L)+L)$

$$L_{21} = \frac{L_{12} L_{22}}{L_{12} + L_{22}}, \quad L_{11} = \frac{L_{12}^2}{L_{12} + L_{22}}, \quad R_{11} = \frac{L_{12}^2 R_{12}}{(L_{12} + L_{22})^2}$$

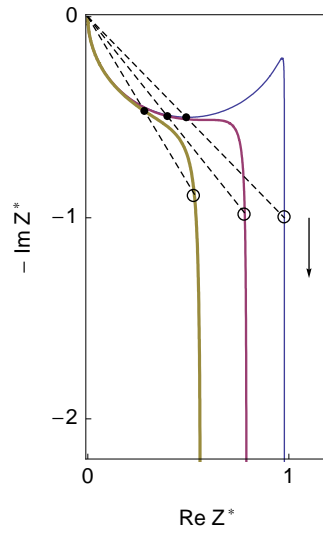


Figure 2.4: Nyquist diagrams of the reduced impedance for the $((R_1+L_2)/L_1)$ circuit (Eq. (2.2), Fig. 2.3, $T = 1/4, 1/9, 1/90$, the line thickness increases with increasing T). Horizontal tangent for $T \leq 1/9$ ($L_1/L_2 \geq 8$). Dots: reduced characteristic angular frequency: $u_{c1} = 1$; circles: reduced characteristic angular frequency $u_{c2} = 1/T$.

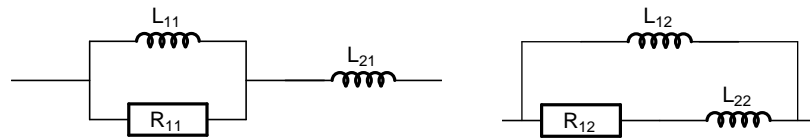


Figure 2.5: The $((R/L)+L)$ and $((R+L)/L)$ circuits are non-distinguishable.