

How to fit transmission lines with ZFit

I – INTRODUCTION

ZFit is the impedance fitting tool of EC-Lab®. This note will describe how to fit transmission lines using one equivalent circuit elements contained in ZFit.

It has been well known for a long time that the Warburg impedance is equivalent to that of a semi-infinite large network i.e. a transmission line, as shown in Fig. 1 [1, 2].

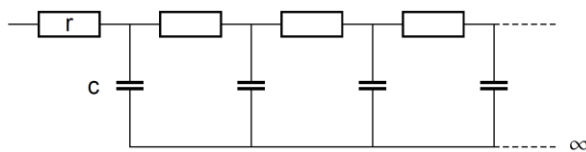


Figure 1: The equivalent circuit of the War-Burg impedance.

More recently it has been shown [3] that the impedance of a L-long transmission line made of χ and ζ elements and terminated by a Z_L element (Fig. 2) is given by the general expression:

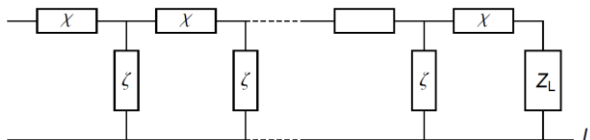


Figure 2: Uniform transmission line made χ and ζ elements and terminated by Z_L [3].

$$Z = \frac{(\zeta\chi - Z_L^2) \operatorname{sh}\left(\frac{L\sqrt{\chi}}{\sqrt{\zeta}}\right)}{Z_L \operatorname{sh}\left(\frac{L\sqrt{\chi}}{\sqrt{\zeta}}\right) + \sqrt{\zeta\chi} \operatorname{ch}\left(\frac{L\sqrt{\chi}}{\sqrt{\zeta}}\right)} + Z_L$$

¹ The transmission lines are named accordingly to the U- $\chi\zeta$ format where U means uniformly distributed and χ and ζ are the elements of the transmission line.

With three limiting cases

- open-circuited transmission line

$$Z_L = \infty \Rightarrow Z = \sqrt{\zeta\chi} \operatorname{coth}\left(\frac{L\sqrt{\chi}}{\sqrt{\zeta}}\right) \quad (1)$$

- short-circuited transmission line

$$Z_L = 0 \Rightarrow Z = \sqrt{\zeta\chi} \operatorname{th}\left(\frac{L\sqrt{\chi}}{\sqrt{\zeta}}\right) \quad (2)$$

- semi-infinite transmission line

$$L \rightarrow \infty \Rightarrow Z = \sqrt{\zeta\chi} \quad (3)$$

Hereafter, some transmission lines are described and the corresponding "simple" equivalent circuit elements are shown. Firstly, the open-circuited transmission lines will be explained, followed by short-circuited and semi-infinite transmission lines¹.

III – OPEN-CIRCUITED TRANSMISSION LINES $Z_L = 1$

II - 1 OPEN-CIRCUITED URC (UNIFORM DISTRIBUTED RC)

Let us consider the open-circuited transmission line made of r and c elements (Fig. 3).

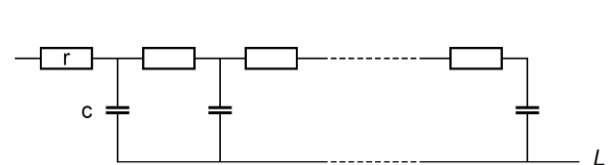


Figure 3: L-long open uniform distributed RC (URC) transmission line [4,5].

Using Eq. (1), the transmission line impedance is given by:

$$\chi = r, \zeta = \frac{1}{j\omega c} \Rightarrow Z = \sqrt{r} \frac{\coth(L\sqrt{rcj\omega})}{\sqrt{cj\omega}} \quad (4)$$

With $\omega = 2\pi f$. This impedance is similar to that of the M element of ZFit

$$Z_M = R_d \frac{\coth\sqrt{\tau_d j\omega}}{\sqrt{\tau_d j\omega}}, R_d = Lr, \tau_d = L^2 rc \quad (5)$$

II - 2 OPEN-CIRCUITED URQ

Replacing c elements by q elements, with

$Z_q = 1/(q(j\omega)^\alpha)$ leads to transmission line shown in Fig. 4.

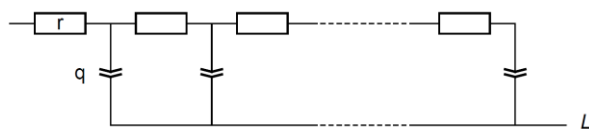


Figure 4: L-long open uniform distributed RQ (URQ) transmission line.

The transmission line impedance is given by

$$\chi = r, \zeta = \frac{1}{q(j\omega)^\alpha}$$

$$\Rightarrow Z = \sqrt{r} \frac{\coth(L\sqrt{rq}(j\omega)^{\alpha/2})}{\sqrt{q}(j\omega)^{\alpha/2}} \quad (6)$$

The impedance is similar to that of the M_a element of ZFit.

$$Z_{M_a} = R \frac{\coth(\tau j\omega)^{\alpha/2}}{(\tau j\omega)^{\alpha/2}} \quad (7)$$

With $R = Lr, \tau = (L^2 rq)^{1/\alpha}$

As an example a Nyquist impedance diagram of a battery Ni-MH 1900 mAh is shown in Fig. 5. The equivalent circuit $R1+L1+Q1/(R2+Ma3)$, containing a M_a element, is chosen to fit the data shown in Fig. 5. The values of the parameters, obtained using the ZFit tool of EC-Lab, are $R1 = 0.049 \Omega$, $L1 = 0.154 \cdot 10^{-6} H$, $Q1 = 0.66 F s^{\alpha-1}$, $\alpha1 = 0.61$, $R2 = 0.0236 \Omega$, $R3 = Lr = 0.057 \Omega$, $\tau3 = (L^2 r q)^{1/\alpha} = 2.25 s$ and $\alpha3 = 0.89$.

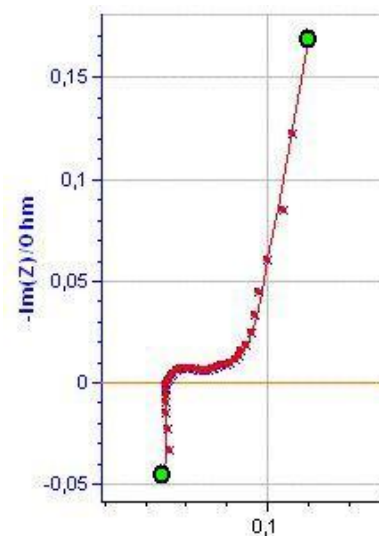


Figure 5: Nyquist impedance diagram of a battery Ni-MH 1900 mAh.

The equivalent circuit of the so-called anomalous diffusion is shown in Fig. 6 [6].

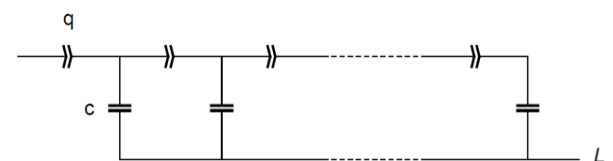


Figure 6: L-long open uniform distributed QC (UQC) transmission line. Anomalous diffusion [6].

The anomalous diffusion impedance is given by

$$\chi = \frac{1}{q(j\omega)^\alpha}, \zeta = \frac{1}{cj\omega}$$

$$\Rightarrow Z = \frac{\coth\left(L\sqrt{\frac{c}{q}}(j\omega)^{\frac{1-\alpha}{2}}\right)}{\sqrt{cq}(j\omega)^{\frac{\alpha+1}{2}}} \quad (8)$$

This impedance is similar to that of the M_g element of ZFit

$$Z_{M_g} = R \frac{\coth(\tau j\omega)^{\gamma/2}}{(\tau j\omega)^{1-\gamma/2}} \quad (9)$$

With $\gamma = 1 - \alpha$, $R = c^{\frac{1-\alpha}{2}} L^{\frac{2-\alpha}{2}} q^{\frac{-1}{2}}$, $\tau = c^{\frac{1}{2}} L^{\frac{2}{2}} q^{\frac{-1}{2}}$.

III – SHORT-CIRCUITED TRANSMISSION LINES $Z_L=0$

III - 1 SHORT-CIRCUITED URRC

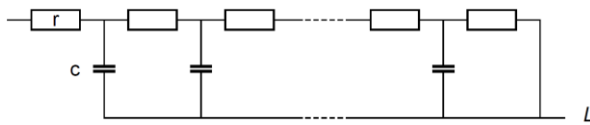


Figure 7: L-long open uniform distributed QC (UQC) transmission line. Anomalous diffusion [6].

Using Eq. (2), the impedance of the short-circuited transmission line made of r and c elements (Fig. 7) is given by

$$\chi = r, \zeta = \frac{1}{cj\omega}$$

$$\Rightarrow Z = r \frac{\text{th}(L\sqrt{rcj\omega})}{\sqrt{rcj\omega}} \quad (10)$$

This impedance is similar to that of the W_d element of ZFit

$$Z_{W_d} = R_d \frac{\text{th}\sqrt{\tau_d j\omega}}{\sqrt{\tau_d j\omega}}, R_d = Lr, \tau_d = L^2 rc \quad (11)$$

IV – SEMI-INFINITE TRANSMISSION LINES: $L \rightarrow \infty$

IV - 1 SEMI-INFINITE URRC

The impedance of the semi-infinite transmission line shown in Fig. 1 is obtained making $L \rightarrow \infty$ in Eq. (10).

$$L \rightarrow \infty \Rightarrow Z = r \frac{\text{th}(L\sqrt{rcj\omega})}{\sqrt{rcj\omega}} \approx \frac{\sqrt{r}}{\sqrt{cj\omega}} \quad (12)$$

This expression is similar to that of the Warburg (W) element of ZFit

$$Z_W = \frac{2\sigma}{\sqrt{j\omega}} \text{ with } \sigma = \frac{\sqrt{r}}{2\sqrt{c}} \quad (13)$$

As an example a Nyquist impedance diagram of a Fe(II)/Fe(III) system is shown in Fig. 8.

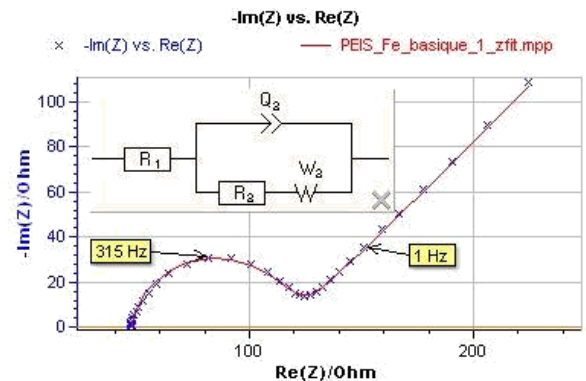


Figure 8: Nyquist impedance diagram of a Fe(III)/Fe(II) system in basic medium.

The Randles circuit $R_1+Q_2/(R_2+W_2)$, containing a Warburg element, is chosen to fit the data shown in Fig. 8. The values of the parameters for equivalent circuit are $R_1 = 47.57 \Omega$, $Q_2 = 17.09 \times 10^{-6} \text{ F s}^{-1}$, $\alpha = 0.885$, $R_2 = 70.94 \Omega$ and $\sigma_2 = 85.33 \Omega \text{ s}^{-1/2}$

$$\Rightarrow \sqrt{\frac{r}{c}} = 42.7 \Omega \text{ s}^{-1/2}.$$

IV - 2 SEMI-INFINITE URRC

First of all, let us calculate the impedance of the L-long URRC transmission line (Fig. 9)

corresponding to diffusion-reaction and diffusion-trapping impedance [7]:

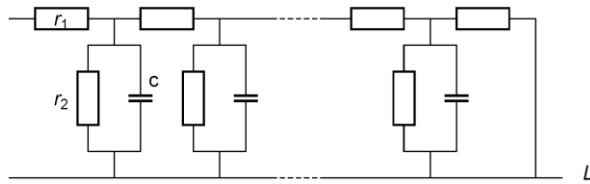


Figure 9: L-long short-circuited uniform distributed RRC (URRC) transmission line.

$$\chi = r_1, \zeta = \frac{r_2}{1 + r_2 c j \omega}$$

$$\Rightarrow Z = \sqrt{r_1 r_2} \frac{\text{th} \left(L \sqrt{\frac{r_1}{r_2} (1 + r_2 c j \omega)} \right)}{\sqrt{1 + r_2 c j \omega}} \quad (14)$$

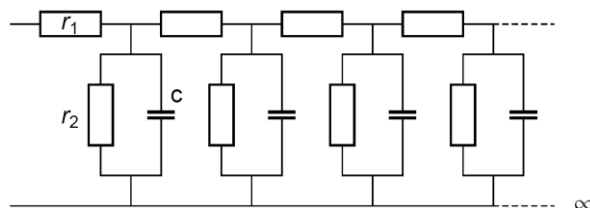


Figure 10: Semi-infinite short-circuited uniform distributed RRC (URRC) transmission line.

With $L \rightarrow \infty$ it is obtained [8]:

$$L \rightarrow \infty \Rightarrow Z \approx \frac{\sqrt{r_1 r_2}}{\sqrt{1 + r_2 c j \omega}} \quad (15)$$

This expression is similar to that of the Gerischer element G of ZFit [9]:

$$Z_G = \frac{R_G}{\sqrt{1 + \tau_G j \omega}}, R_G = \sqrt{r_1 r_2}, \tau_G = r_2 c \quad (16)$$

IV - 3 SEMI-INFINITE URRQ

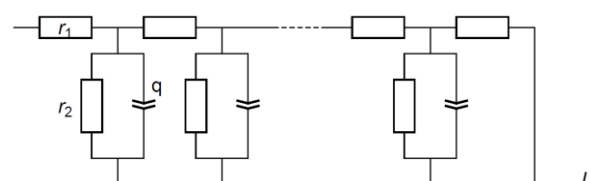


Figure 11: L-long short-circuited uniform distributed RRQ (URRQ) transmission line.

Replacing c elements by q elements

$$\chi = r_1, \zeta = \frac{r_2}{1 + r_2 c (j \omega)^\alpha}$$

$$\Rightarrow Z = \sqrt{r_1 r_2} \frac{\text{th} \left(L \sqrt{\frac{r_1}{r_2} (1 + r_2 c (j \omega)^\alpha)} \right)}{\sqrt{1 + r_2 c (j \omega)^\alpha}} \quad (17)$$

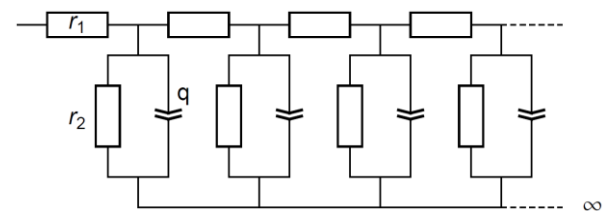


Figure 12: Semi-infinite short-circuited uniform distributed RRQ (URRQ) transmission line.

And $L \rightarrow \infty \Rightarrow Z \approx \frac{\sqrt{r_1 r_2}}{\sqrt{1 + \tau (j \omega)^\alpha}} \quad (18)$

This expression is similar to that of the G_a element of ZFit

$$Z_{G_a} = \frac{R}{\sqrt{1 + \tau (j \omega)^\alpha}}, R = \sqrt{r_1 r_2}, \tau = r_2 q \quad (19)$$

V – CONCLUSION

Seven elements, W, Wd, M, Ma, Mg, G and G_a , available in ZFit correspond to different transmission lines (Tabs. I and II).

Table I: Summary table.

Transmission line	ZFit Element	
Open Circuited	URC	M
	URQ	Ma
	UQC	Mg
Short circuited	URC	Wd
Semi-infinite	URC	W
	URRC	G
	URRQ	G_a

Data files can be found in :

C:\Users\xxx\Documents\EC-Lab\Data\Samples\EIS\PEIS_Fe_Basique_1

and

AN43_peis_batteries_carouf_01_PEIS_C06

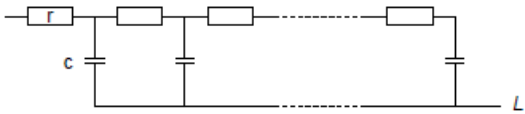
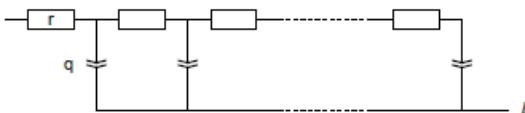
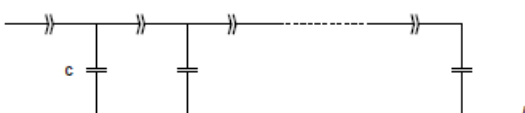

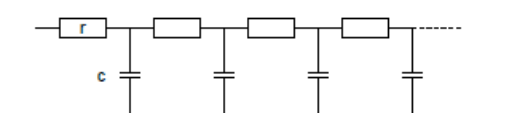
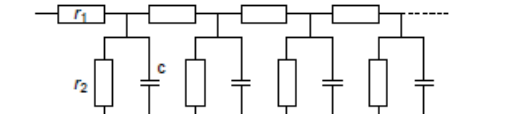
REFERENCES

- 1) J. C. Wang, J. Electrochem. Soc., 134 (1987) 1915.
- 2) M. Sluyters-Rehbach, Pure & Appl. Chem., 66 (1994) 1831.
- 3) J. Bisquert, Phys. Chem. Chem. Phys., 2 (2000) 4185.
- 4) G. C. Temes and J. W. Lapatra, *Introduction to Circuits Synthesis and Design*, McGraw-Hill, New-York, 1977.

- 5) J.-P. Diard, B. Le Gorrec, and C. Montella, J. Electroanal. Chem., 471 (1999) 126.
- 6) J. Bisquert and A. Compte, J. Electroanal. Chem., 499 (2001) 112.
- 7) J.-P. Diard and C. Montella, J. Electroanal. Chem., 557 (2003) 19.
- 8) B. A. Boukamp and H. J.-M. Bouwmeester, Solid State Ionics 157 (2003) 29.
- 9) H. Gerischer, Z. Physik. Chem. (Leipzig), 198 (1951) 286.

Revised in 11/2018

Table II: ZFit elements vs. transmission lines

ZFit element	Equations	Transmission line
M	$R_d \frac{\coth \sqrt{\tau_d j \omega}}{\sqrt{\tau_d j \omega}}$ $R_d = L r, \tau_d = L^2 r c$	
M _a	$R \frac{\coth(\tau j \omega)^{\alpha/2}}{(\tau j \omega)^{\alpha/2}}$ $R = L r$ $\tau = (L^2 r q)^{1/\alpha}$	
M _g	$R \frac{\coth(\tau j \omega)^{\gamma/2}}{(\tau j \omega)^{1-\gamma/2}}$ $R = c^{\frac{1}{\gamma}-1} L^{\frac{2}{\gamma}-1} q^{-1/\gamma}$ $\tau = c^{\frac{1}{\gamma}} L^2 / \gamma q^{-1/\gamma}$	
W _d	$R_d \frac{\text{th} \sqrt{\tau_d j \omega}}{\sqrt{\tau_d j \omega}}$ $R_d = L r$ $\tau_d = L^2 r c$	
W	$\frac{2 \sigma}{\sqrt{j \omega}}$ $\sigma = \frac{\sqrt{r}}{2 \sqrt{c}}$	
G	$\frac{R_G}{\sqrt{1 + \tau_G j \omega}}$ $R_G = \sqrt{r_1 r_2}$ $\tau_G = r_2 c$	
G _a	$\frac{R_G}{\sqrt{1 + \tau_G (j \omega)^\alpha}}$ $R_G = \sqrt{r_1 r_2}$ $\tau_G = r_2 q$	